

Digital Integrated Circuits

Lab 2

Inverter Simulation

Dr. Yanan Sun

Email: sunyanan@sjtu.edu.cn

Office: Rm 416-2, Building of Microelectronics

2025/10/21

Outline


- Hspice
- Lab Contents
- Report Requirements

Outline

- Hspice
- Lab Contents
- Report Requirements


常用激励源 — 脉冲电压源

 Vxxx n+ n- pulse/pu <(> V1 V2 <td<tr<tf<pw<per>>>>
<)>



➤ 示例: `Vin 1 0 PULSE (0V 5V 10ns 10ns 10ns 40ns 100ns)`

 定义了一个低电平为 0V，高电平为 5V，延迟为 10ns，脉冲上升延迟10ns，下降延迟 10ns，脉冲宽度 40ns，周期为 100ns 的脉冲信号电压源



上升/下降时间、延时测量

□ TRIG 和 TRAG 可以配合.MEASURE 语句测量特定事件发生之间的延迟

.MEASURE <DC|AC|TRAN> result TRIG ... TARG ... <MINVAL=val> <WEIGHT=val>


示例:

.MEASURE TRAN tpLH

+ TRIG V(a) VAL='SUPPLY/2' FALL=1

+ TARG V(b) VAL='SUPPLY/2' RISE=1

 本示例测量了从 a 节点第一次在下降沿中达到 SUPPLY/2 开始，到 b 节点第一次在上升沿中达到 SUPPLY/2 结束间的延迟时间。



上升/下降时间、延时测量 (cont.)

▣ TRIG 和 TRAG 可以配合.MEASURE 语句测量特定事件发生之间的延迟

.MEASURE <DC|AC|TRAN> result TRIG ... TARG ... <MINVAL=val> <WEIGHT=val>

示例:

```
.meas TRAN Trise
```

```
+ TRIG v(out) VAL='Vmin+0.1*Vmax' RISE=1
```

```
+ TARG v(out) VAL='0.9*Vmax' RISE=1
```

```
.meas TRAN Tfall
```


```
+ TRIG v(out) VAL='0.9*Vmax' FALL=2
```

```
+ TARG v(out) VAL='Vmin+0.1*Vmax' FALL=2
```

```
.meas TRAN Tdelay
```

```
+ TRIG v(in) VAL=2.5 FALL=1
```

```
+ TARG v(out) VAL=2.5 FALL=2
```

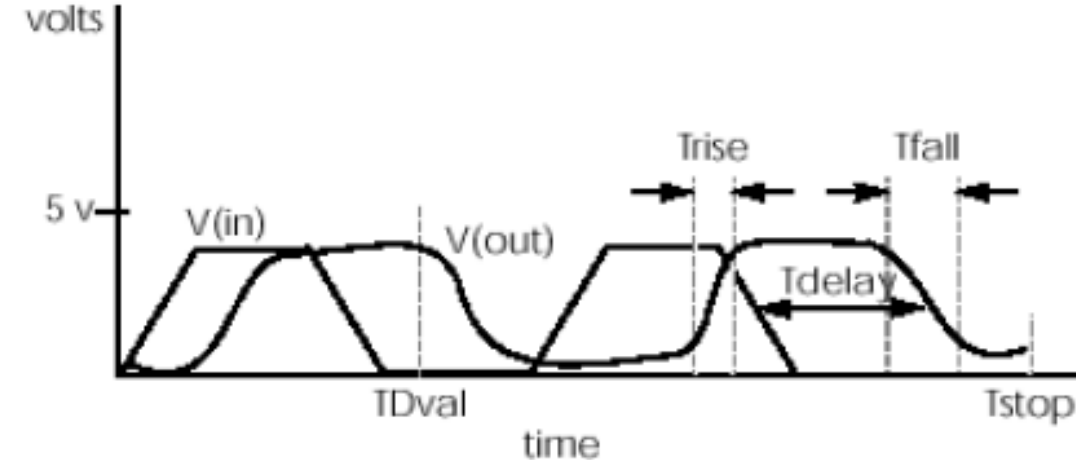

功耗测量

❑ HSPICE can measure power

- Instantaneous $P(t)$
- Or average P over some interval

```
.print P(vdd)  
.measure pwr AVG P(vdd) FROM=0ns TO=10ns
```

⇒ **测量电压源 Vdd 在 0ns-100ns 间的平均功耗**

❑ Power in single gate

- Connect to separate V_{DD} supply
- Be careful about input power

输入控制语句 .DATA

□.data

- 基于数据驱动的分析允许用户修改任意数量的参数。
- 可以系统罗列需要分析扫描的参数列表。

```
* Inline .DATA example
.Tran 1n 100n SWEEP DATA=devinf
.AC DEC 10Hz 100kHz SWEEP DATA=devinf
.DC TEMP -55 125 10 SWEEP DATA=devinf
*
.DATA devinf Width Length Vth Cap
+          10u  100u  2v  5p
+          50u  600u 10v 10p
+          100u 200u  5v 20p
.ENDDATA
```

```
* Multiline .DATA example
.PARAM Vds=0 Vbs=0 L=1.0u
.DC DATA=vdot
..DATA vdot
Vbs      Vds      L
+0        0.1      1.0u
+0        0.1      1.5u
+-1       0.1      1.0u
+0        0.5      1.0u
.ENDDATA
```


DATA Statement: Inline or Multiline

Outline





- Hspice
- Lab Contents
- Report Requirements

 Device Models for Inverter Simulation

- ❑ Use the Predictive Technology Model (PTM) to evaluate the DC characteristics of ptm16hp FinFETs
 - PTM model is released in Lab section
 - Use the high-power (HP) models
 - For both n-channel and p-channel devices



Lab_LIB > FINFET > modelfiles > hp

 16nfet.pm	2012/5/31 15:14	Perl Module 源文件	11 KB
 16pfet.pm	2012/5/31 15:14	Perl Module 源文件	11 KB
 20nfet.pm	2012/5/31 15:14	Perl Module 源文件	11 KB
 20pfet.pm	2012/5/31 15:14	Perl Module 源文件	11 KB



FinFET

Simulation Settings

- ❑ $L_g = 20\text{nm}$ for ptm16hp FinFETs
- ❑ Supply voltage is 0.75V for FinFETs
- ❑ Simulation temperature
 - $T = 25^\circ\text{C}$

 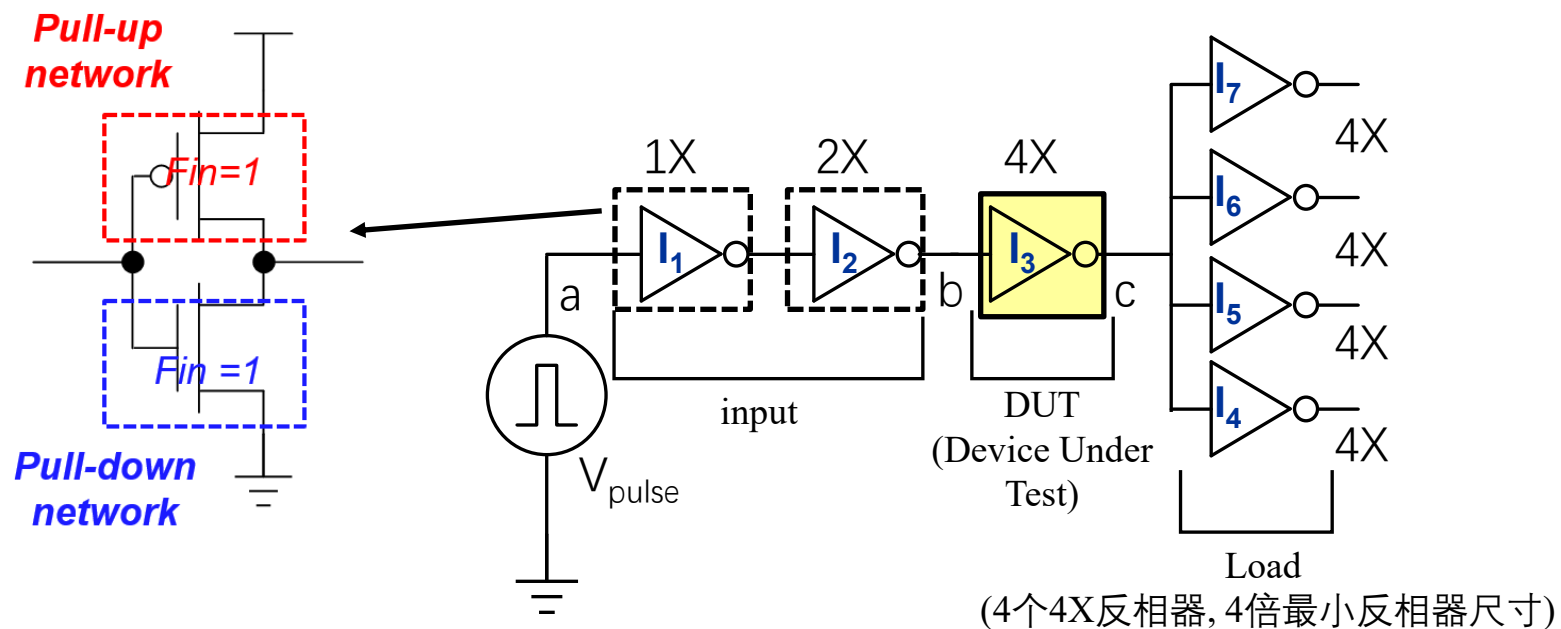Task 1: CMOS Inverter FO4 Delay Measurement

- Measure FO4 delay (t_{pLH} , t_{pHL} , t_p) of inverter




$$t_p = \frac{t_{pLH} + t_{pHL}}{2}$$

Vpulse	Value
V1	0V
V2	0.75V
Delay Time	400ps
Raise Time	25ps
Fall Time	25ps
Pulse Width	400ps
Period	800ps

Task 1: 语法提示

❑ Trapezoidal pulse : pulse

 

PULSE (v2 v1 td tr tf pw per)

e.g. VIN in 0 PULSE 0 5 2ns 2ns 2ns 30ns 80ns

❑ Measure delay

You can use the .MEASURE command to measure the propagation delay


For example (measure the propagation delay from b to c for L->H transition):

```
.MEASURE TRAN tpLH  
+ TRIG V(b)='0.5*SUPPLY' FALL=2  
+ TARG V(c)='0.5*SUPPLY' RISE=2
```

❑ Use function to measure tp


```
.measure tran tp param='(TpLH+TpHL)/2'
```

$$t_p = \frac{t_{pLH} + t_{pHL}}{2}$$

 

 Task 2: Delay Optimization for Inverter Chain

- For an inverter chain with 4 stages and $256 \times C_{\text{load}}$, find the minimum delay chain design



- Design the optimum delay chain by FinFET technology

Hint:

- For a given stage N , the optimum f is determined by $f = \sqrt[N]{F}$
- Note that the sizes of FinFETs should be integer number
- Different rounding method may induce different results

Task 2: 语法提示


❑ Multi-points sweep

Hint: The first inverter's fin number is one. And you can use parameters to represent the fin numbers of the following three inverters and sweep their different combinations.

*For example, suppose the following three inverter has fin number of s1,s2,s3

```
.tran 1ps 10ns sweep data=datam
```


```
.data datam s1 s2 s3  
4 16 64  
4 15 60  
4 20 80  
.enddata
```

 

 Task 3: CMOS Inverter Power

❑ Measure the power of inverter chain

- Only include the power consumption of inverter chain
- Apply a pulse voltage on the input node and measure the power averaging for multiple cycles



The chain size should use the optimum values you have found

- You can use two different power supply sources for the DUT inverter and other parts (for example, use V_{DD1} for the DUT inverter while using V_{DD2} for the other parts, if you have)
- The power consumption of the load part does not need to be included in the power consumption of the inverter chain under test.

Task 3: 语法提示

❑ Measure power

Hint: You can use the .MEASURE command to measure the power consumption

```
.MEASURE <DC|AC|TRAN> result func out_var FROM=val TO=val
```

*For example (measure the energy of the circuit from VDD)

```
.MEASURE TRAN avgpower AVG P(VDD) FROM=1ns TO=80ns
```

❑ The power consumption measurement may be negative because the current direction is flowing out of VDD.

Task 4: EDP measurement


□ Using optimized chain to find optimal point of Energy and delay

Power-Delay Product (PDP):

$$PDP = P_{av} t_p$$

Energy-Delay Product (EDP):
 
$$EDP = PDP * t_p = P_{av} t_p^2 = \frac{C_L V_{DD}^2}{2} t_p$$



Hint:

- To find ensure your results, you can sweep the VDD beyond the standard supply
- Ultralow VDD may result in unfunctional circuit


□ Use function to measure EDP

```
.measure tran edp param='abs(avgpower*tp*tp)'
```

 Task 5 (Optional): Inverter chain optimization with unfixed stages

□ For a given Initial stage and Cload, find the minimum delay chain design

Optimize Stage Number and Size of each stage



□ Design the optimum delay chain by FinFET technology

Hint:

- For a given stage N, the optimum f is determined by $f = \sqrt[N]{F}$
- Sweep the N to find corresponding f
- In theory, the optimum f should satisfy

$$C_L = F \cdot C_{in} = f^N C_{in} \quad \text{with} \quad N = \frac{\ln F}{\ln f} \quad C_{int} = \gamma C_g$$

$$f = \exp(1 + \gamma/f)$$

Outline

- Hspice
- Lab Contents
- Report Requirements

Report Requirement

- ❑ Write your lab report like writing a technical document (readable, comprehensive analysis, no typo...)
- ❑ You may include
 - Introduction/background
 - Lab procedures
 - Lab results
 - **Technical analysis of the simulation results**
 - Observations and conclusions

Submission

☐ You need to submit your report and code

- Name of report (in PDF format): **lab2_report_[Name]_[Student No.].pdf**
- Name of code (compressing the files):
lab2_code__[Name]_[Student No.].zip

☐ Please upload your report to Canvas course website

☐ Submission of lab2 report and code will be due on

4th November 2025